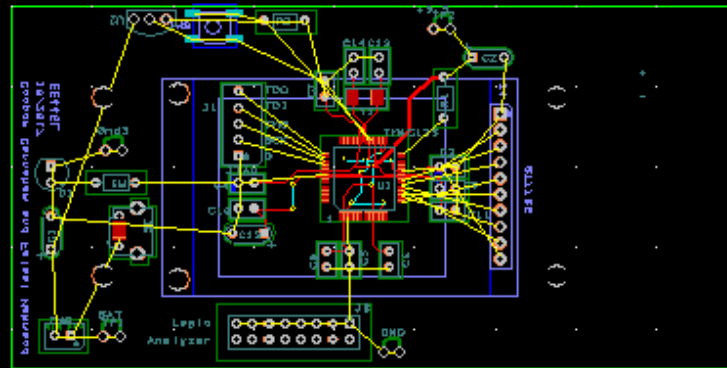


Information to add to PCB


Your name	Casper and Foteel
Project name	EE445L Design Lab
Board Part Number	UTX-2817@ISM

University of Texas at Austin







早市

Power

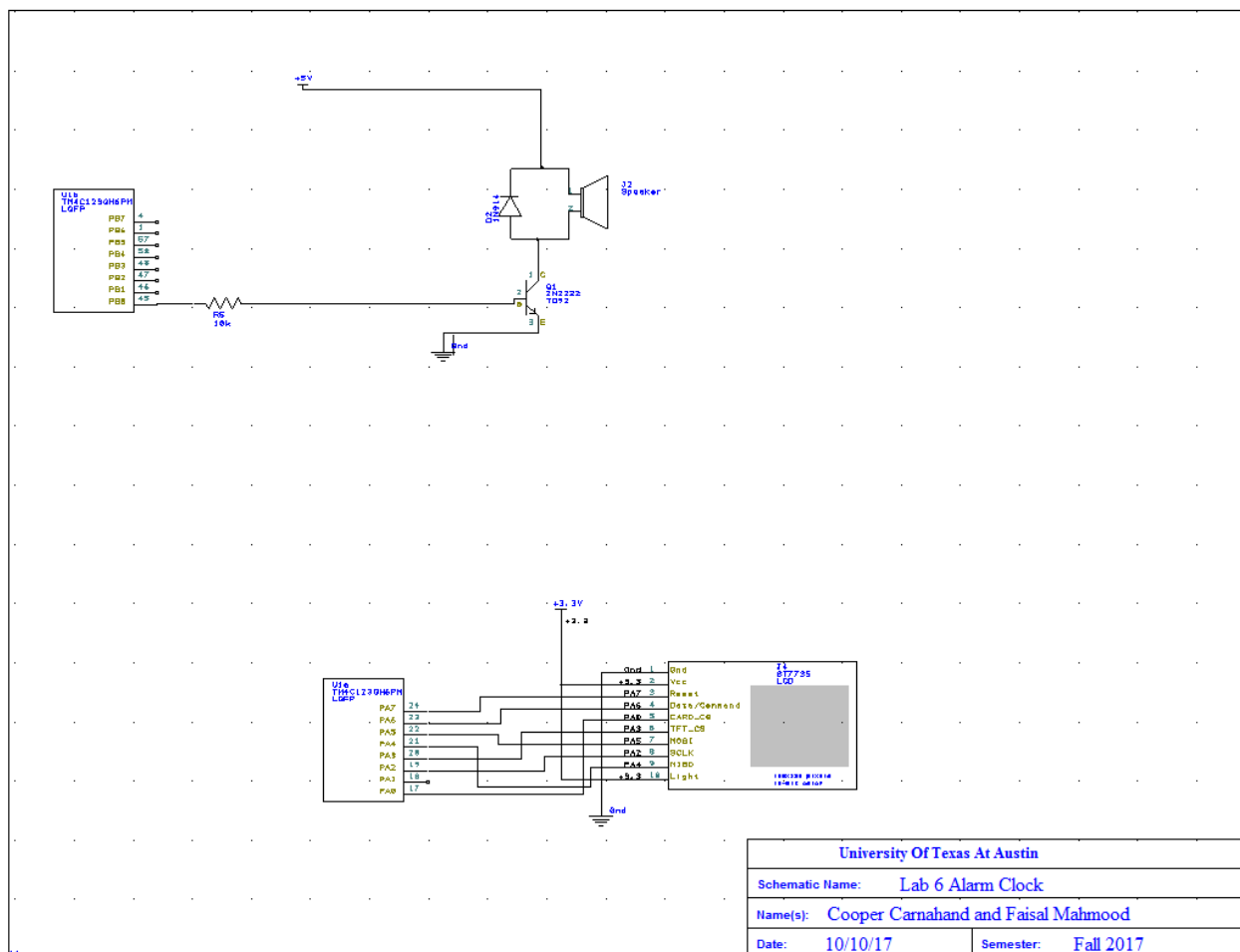

University Of Texas At Austin	
Schematic Name:	Lab 6 Alarm Clock
Name(s):	Cooper Carnahand and Faisal Mahmood
Date:	10/10/17
Semester:	Fall 2017

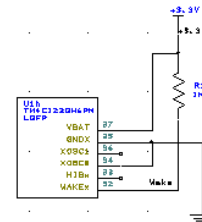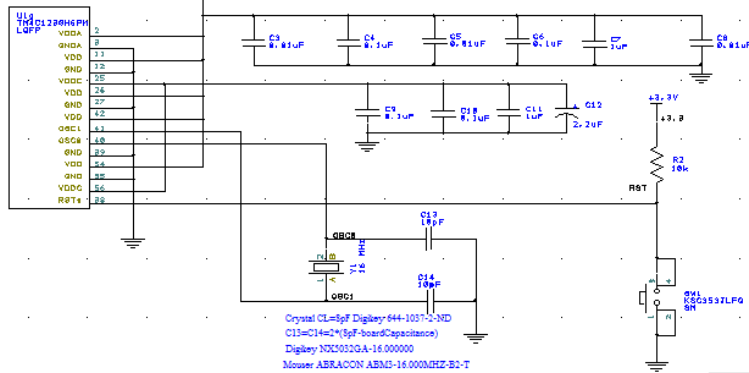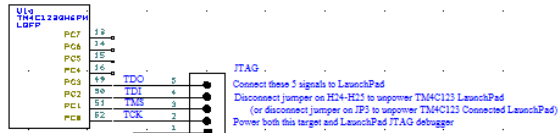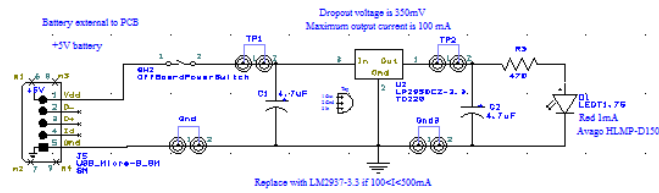

University Of Texas At Austin

Schematic Name: Lab 6 Power Clock JTAG

Name(s): Cooper Carnahan

Date: 10/10/17

Semester: Fall 2017

